

Using Sipex PWM Controllers for Boost Conversion

Introduction:

Sipex PWM controllers can be configured in boost mode to provide efficient and cost effective solutions. Circuit operation and design procedure are explained in the following.

Circuit Operation:

A boost circuit using Sipex's SP6136 controller is shown in figure 1. When MOSFET M1 is on, inductor L1 gets charged while the output capacitor sustains the load current. When M1 turns off, L1 replenishes the capacitor's charge through D1. Under light load conditions, the energy stored in the inductor is discharged before the next switching cycle begins (i.e., inductor current reduces to zero). This is referred to as Discontinuous Conduction Mode (DCM).

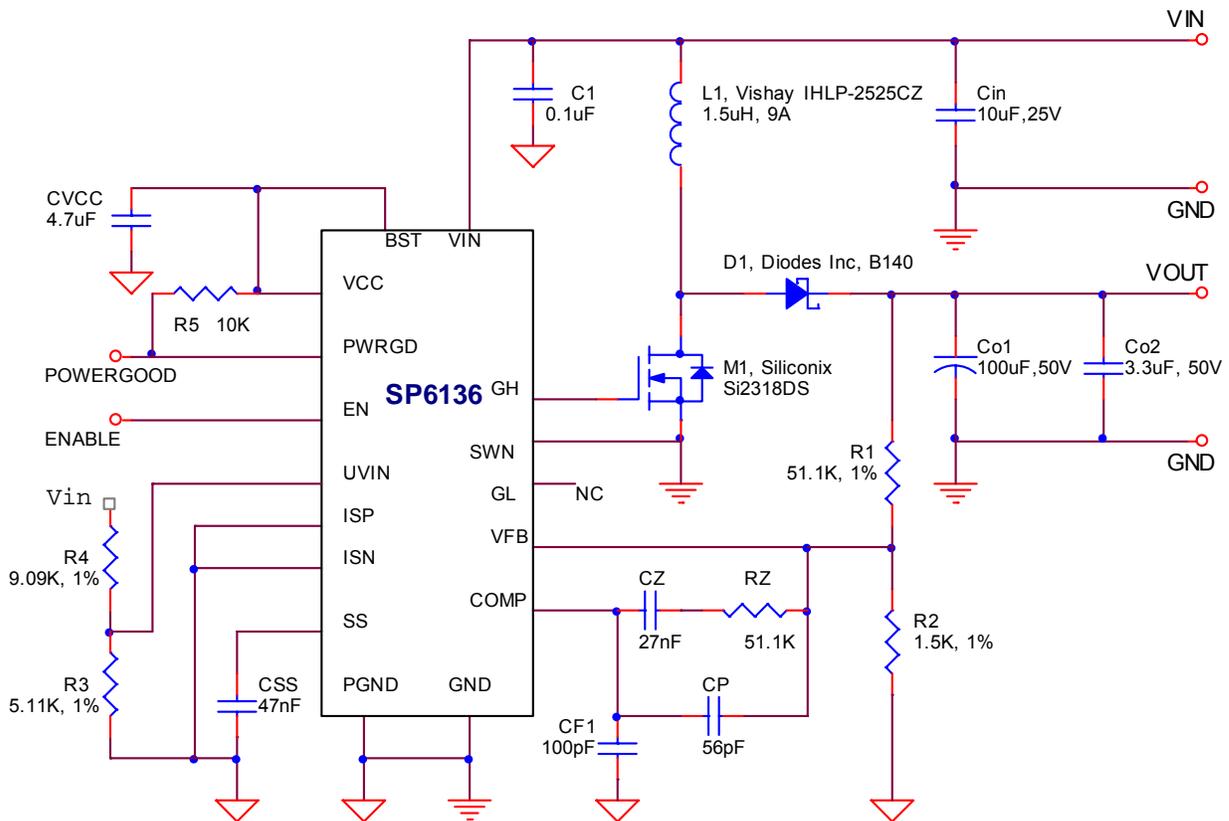


Figure 1- Boost converter based on SP6136, $V_{IN}=7$ to $18V$, $V_{OUT}=28V$, $I_{OUT}=0$ to $0.5A$, converter operates at Discontinuous Current Mode under all line and load conditions

Design Strategy:

As far as Conduction Mode is concerned, there are basically two choices in designing a boost converter:

1- Design for Discontinuous Conduction Mode (DCM) over full operating conditions: This approach offers easy control of the boost converter. With DCM, the converter transfer function has a single pole (second pole and Right Half Plane (RHP) zero are insignificant). Peak current (and IRMS) however, will be high at low VIN and/or high load conditions.

2- Design for Continuous Conduction Mode (CCM) for nominal operating conditions: With this approach the converter will transition to DCM at light loads. An RHP zero is present and hence, compensation is more difficult. The inductor current ripple, however, is significantly reduced.

DCM Boost Design Procedure:

For cases where output current requirement is low, less than 2A, a DCM design can be used as follows:

1- Controller selection

Sipex offers controllers with fixed operating frequency ranging from 300KHz to 2.5MHz. 600Khz controllers such as SP6136 and SP6134 offer a good compromise. This intermediate switching frequency helps reduce inductor size without incurring significant switching losses in the MOSFET M1. SP6134 is recommended for battery operated applications. This controller requires external VCC, which can be shut down -- removing VCC results in very low leakage current. SP6136 is recommended for applications where external VCC is not available.

2- Inductor L1

Select an inductor based on required inductance (L1) and peak current (Ip). The following calculations assume that in order to ensure DCM operation a dead-time of 20% of full switching period is needed [1]. Hence, the combined conduction time of the MOSFET and diode is 80% of the switching period. This is the reason for K=0.8 used in following equations.

Calculate the required inductance from:

$$L1 = \frac{K \times \frac{Vo}{Io} \times Ton}{2 \times \left(\frac{Vo}{Vin, \min} \right)^2} \dots\dots\dots (1)$$

Where:

K = 0.8 is ratio of MOSFET and diode conduction time to T (T=1/f)

$\frac{Vo}{Io}$ is output impedance at full load Io

Vo is output Voltage

Vin,min is minimum input Voltage

Ton is maximum on time of MOSFET M1.

Calculate TON from:

$$T_{on} = \frac{0.8 \times \frac{1}{f} \times (V_o - V_{in, \min})}{V_o} \dots\dots\dots (2)$$

Calculate peak inductor current Ip from:

$$I_p = T_{on} \times \frac{V_{in, \min}}{L1} \dots\dots\dots (3)$$

Where:

TON is the maximum on time of the MOSFET calculated above

L1 is the inductance calculated above

3- MOSFET M1

Choose M1 based on Voltage rating (BVdss), current rating (Ids), ON resistance rating RDS(ON)) and gate charge (Qg). BVdss must be greater than Vo of the converter. M1 must have the current capability to conduct Ip calculated in step 2. RDS(ON)) can be up to twice the DCR of L1. Select a MOSFET with lowest Qg that meets the above requirements.

4- Schottky diode D1

Select D1 based on the reverse blocking Voltage (VR) and forward current (IF). VR must meet the output Voltage requirement of the converter and IF must meet the peak current requirement Ip calculated in step 2.

5- Input capacitor CIN

Select CIN based on input Voltage requirement, RMS ripple current rating and capacitance.

Calculate input rms current from equation for triangular current waveform:

$$I_{rms} = I_p \sqrt{\frac{0.8}{3}} \dots\dots\dots (4)$$

Where 0.8 is combined conduction time of the MOSFET and diode as explained in step 2 and Ip is peak inductor current also calculated in step 2. Since peak inductor current is supplied by the input capacitor, it is used for calculating IRMS for CIN.

Calculate capacitance from:

$$C_{in} = I_{rms} \times \frac{T - T_{on}}{0.2 \times V} \dots\dots\dots (5)$$

Where T and TON are defined in step 2 of the procedure

6- Output capacitor COUT

For optimum performance use a combination of ceramic and electrolytic capacitors. A ceramic capacitor with its low ESR helps reduce output Voltage ripple.

A larger electrolytic capacitor is needed to keep a stiff output Voltage. The choice of this capacitor is critical since it dictates the frequency of converter's single pole (see section 7). In addition, its ESR introduces a "Zero" that limits system bandwidth. As a rule of thumb, select a 100uF low ESR capacitor and calculate the uncompensated transfer function and adjust the capacitance value if necessary.

7- Feedback loop compensation

The Control-to-Output transfer function of the converter is shown in figure 2. This is also referred to as an "uncompensated transfer function". The converter has essentially a single pole transfer function due to DCM. Pole frequency f_p is determined by C_{OUT} . V_{IN} and I_{OUT} influence f_p (and therefore crossover frequency f_c) as shown in figure 2. There is a "Zero" due to ESR of Aluminum Electrolytic C_{OUT} . Use the equations of appendix 1 to plot this transfer function. Then use a type II compensator to increase the cross-over frequency and increase the low-frequency gain.

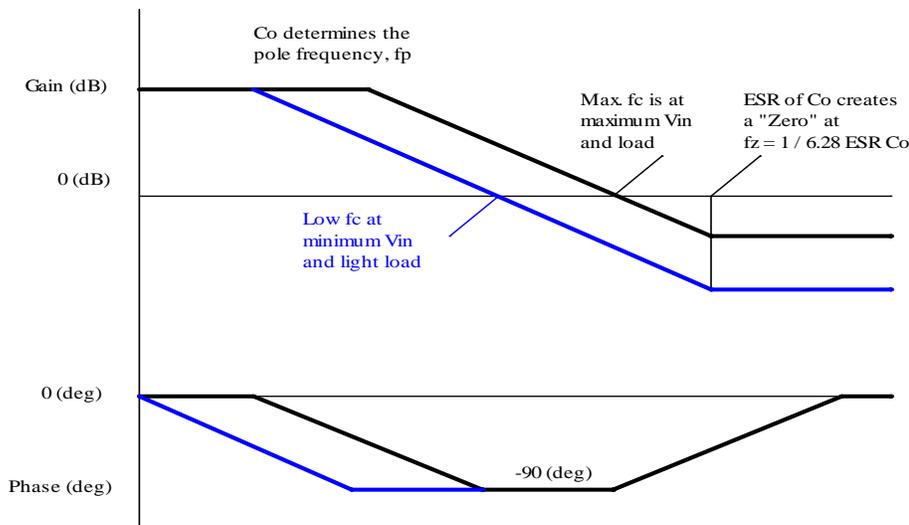


Figure 2- Control-to-Output transfer function of DCM boost converter, Gain/phase corresponding to low V_{IN} and light load are shown in blue.

Design example:

Design a boost converter that will meet the following requirements: $V_{IN} = 7V$ to $18V$ with nominal value of $12V$, $V_{OUT} = 28V$, $I_{OUT} = 0.5A$. An external V_{CC} is not available for this design.

Following the design procedure outlined in the previous page:

1- Use Sipex SP6136 for controller.

2- Calculate the required inductance for L1

First calculate the T_{ON} of M1 from (2)

$$T_{on} = \frac{0.8 \times \frac{1}{600000 \text{ Hz}} \times (28V - 7V)}{28V}$$

$T_{ON} = 1\mu s$, then use (1) to calculate L1

$$L1 = \frac{0.8 \times \frac{28V}{0.5} \times 1\mu s}{2 \times \left(\frac{28V}{7V}\right)^2}$$

$L1 = 1.4 \mu H$ (use a $1.5\mu H$ standard value)

Calculate peak inductor current from (3)

$$I_p = 1\mu s \times \frac{7V}{1.5\mu H}$$

$I_p = 4.67A$

Choose a $1.5\mu H$ inductor that meets this current rating. As an example Vishay's IHLP-2525CZ-1R5 can be used ($L=1.5\mu H$, $DCR=15m\Omega$, $I=9A$, size= $6.47 \times 6.86 \times 3mm$).

3- Select a $40V$ rated MOSFET that has a $4.67A$ peak current rating. For example Siliconix's Si2318DS can be used ($BV_{dss} = 40V$, $R_{DS(ON)} = 58m\Omega$, $I_d=3.5A$ (continuous), $Q_g=10nC$).

4- Select a $40V$ rated Schottky that has a $4.67A$ peak current capability (ex. Diodes Inc B140).

5- Use $25V$ ceramic input capacitor and calculate required I_{RMS} and C_{IN} from (4) and (5) respectively:

$$I_{rms} = 4.67 A \times \sqrt{\frac{0.8}{3}}$$

$I_{RMS} = 2.41$

$$C_{in} = 2.41 A \times \frac{1.67 \mu s - 1\mu s}{0.2V} = 8.1\mu F$$

Use a $10\mu F$, $25V$ ceramic capacitor

6- Use a low ESR 100uF, 50V Aluminum electrolytic (ex., Sanyo 50MV1000WX). The low ESR helps maximize the “Zero” frequency (see figure 3). Use a 3.3uF ceramic in parallel to help reduce output ripple.

7- Feedback loop compensation

Using the procedure outlined in appendix 1, the control-to-output transfer function is calculated and plotted in figure 3. Using an Error Amplifier (EA) with type II compensation as shown in figure 4, it is desirable to increase the cross-over frequency f_c shown in figure 3 to a maximum of 1/5 of switching frequency f_s . In this example, however, f_c cannot be increased due to the ESR zero. In order to leave f_c unchanged, compensation should have a gain of 0dB, hence $RZ=R1=51.1K\Omega$. Place compensator “Zero” at Max $f_p=108Hz$. Since RZ is already set at 51.1K Ω , then $CZ=28nF$ (use 27nF). Set the compensator pole at a sufficiently low frequency to obtain good noise attenuation at the given switching frequency. For example, in order to obtain a 20dB attenuation at 600kHz, set the pole frequency to 60KHz. Solving for C_P , we get $C_P=52pF$ (use 56pF).

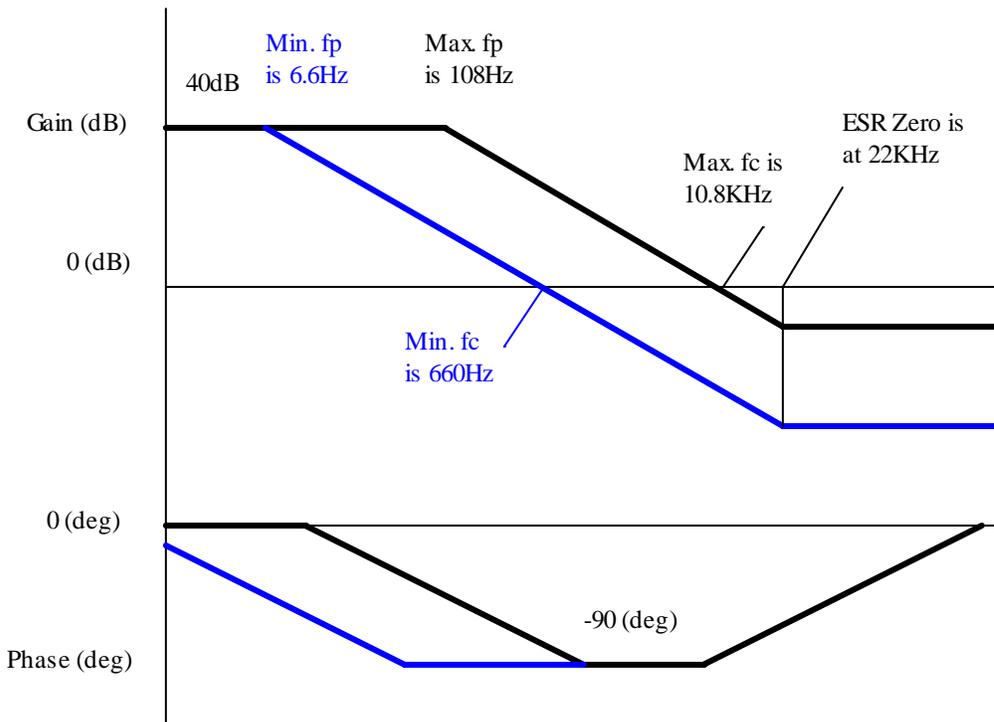


Figure 3- Design example Control-to-output transfer function, gain/phase corresponding to $V_{IN}=7V$ and $I_o=50mA$ are shown in blue.

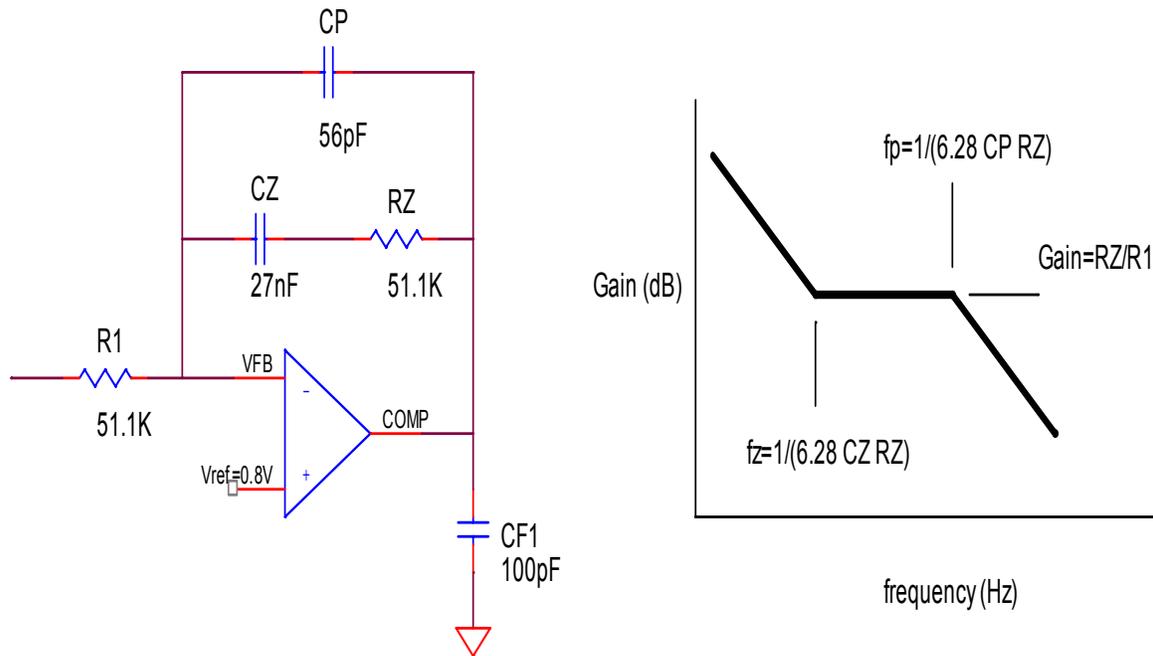


Figure 4- Error Amplifier (EA) and its transfer function for type II compensation, components shown are redrawn from figure 1, Error Amplifier is internal to SP6136 controller.

8-Miscellaneous

Select Voltage divider resistors as follows:

Let $R2 = 1.5K\Omega$ then

$$R1 = R2 \times \left[\left(\frac{V_{out}}{V_{ref}} \right) - 1 \right]$$

$$R1 = 1.5K \times \left[\left(\frac{28V}{0.8V} \right) - 1 \right]$$

$R1 = 51K$ (select $51.1K\Omega$ standard)

Select Under Voltage Lock Out resistors for $V_{IN}(\text{start}) = 7V$ according to the procedure given in the data sheet. Choosing $R3 = 5.11K\Omega$ then $R4 = 9.09K\Omega$.

Other small signal components, shown in figure 1, are standard components required for the operation of the SP6136.

[1] *Switching Power Supply Design*, A. Pressman, pages 27, 30.

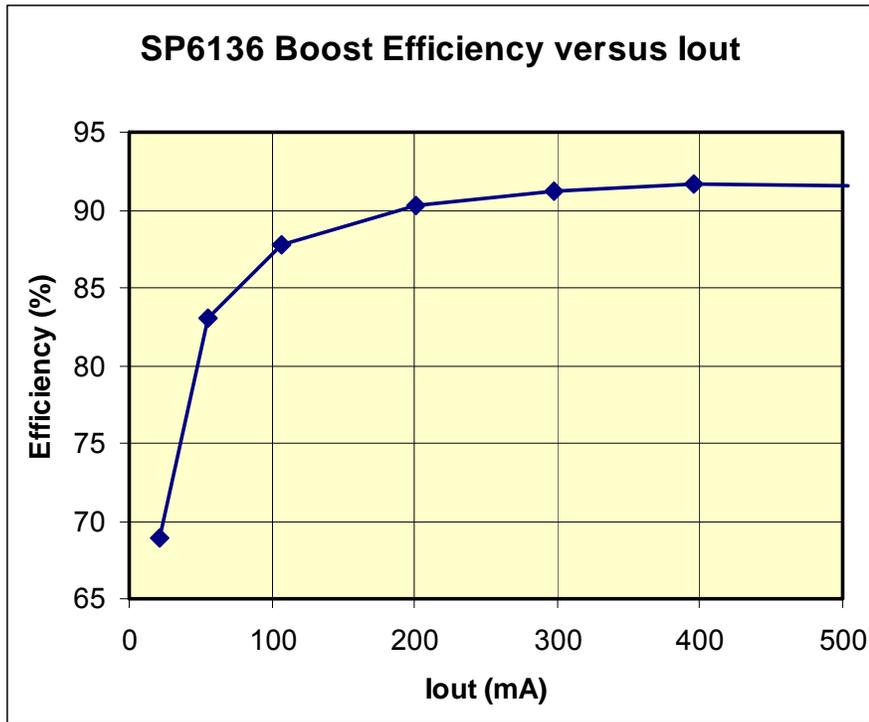


Figure 5- Efficiency at V_{IN}=12V

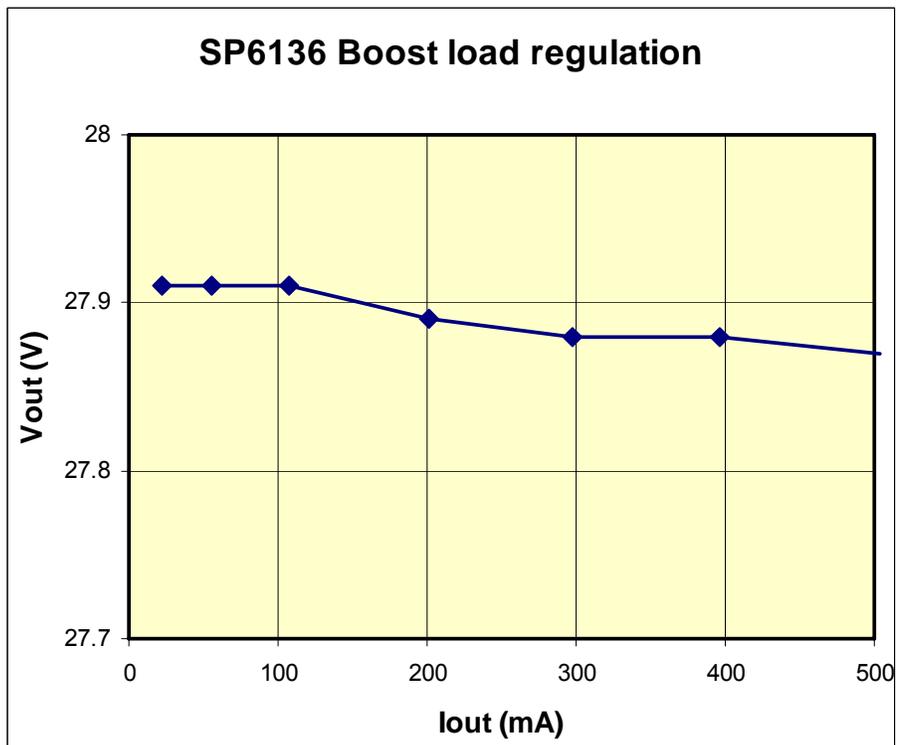


Figure 6- Load regulation at V_{IN}=12V

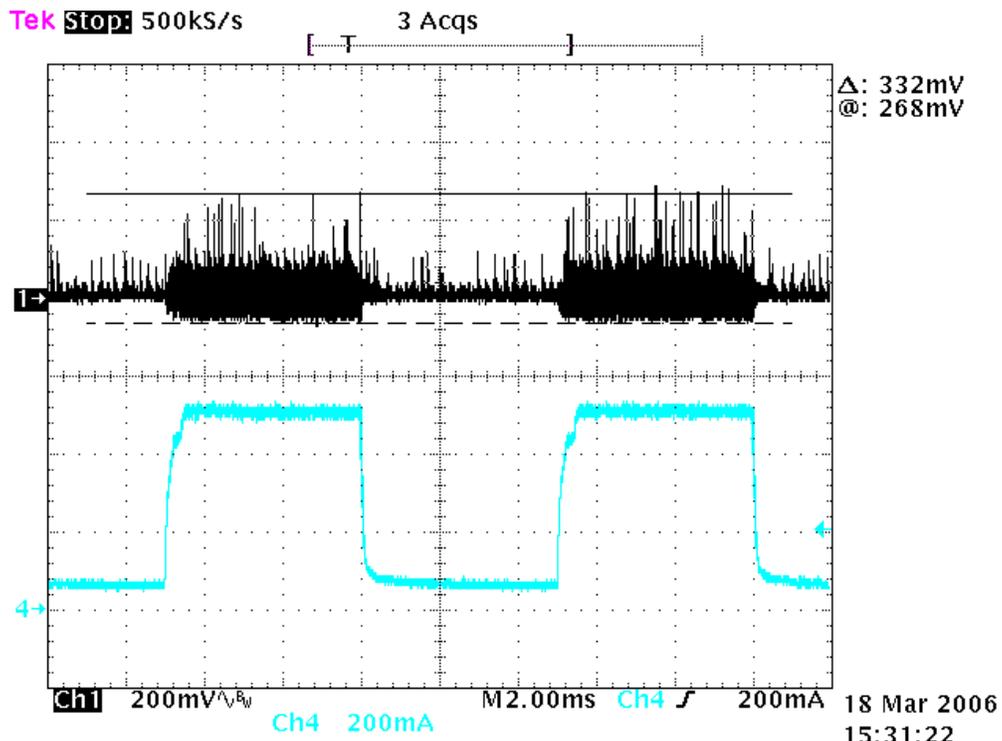


Figure 7- Step load response, $I_1=50\text{mA}$, $I_2=500\text{mA}$, $f=1\text{KHz}$, $D=0.5$, $\text{Ch1}=\text{V}_{\text{OUT}}$, $\text{Ch4}=\text{I}_{\text{OUT}}$

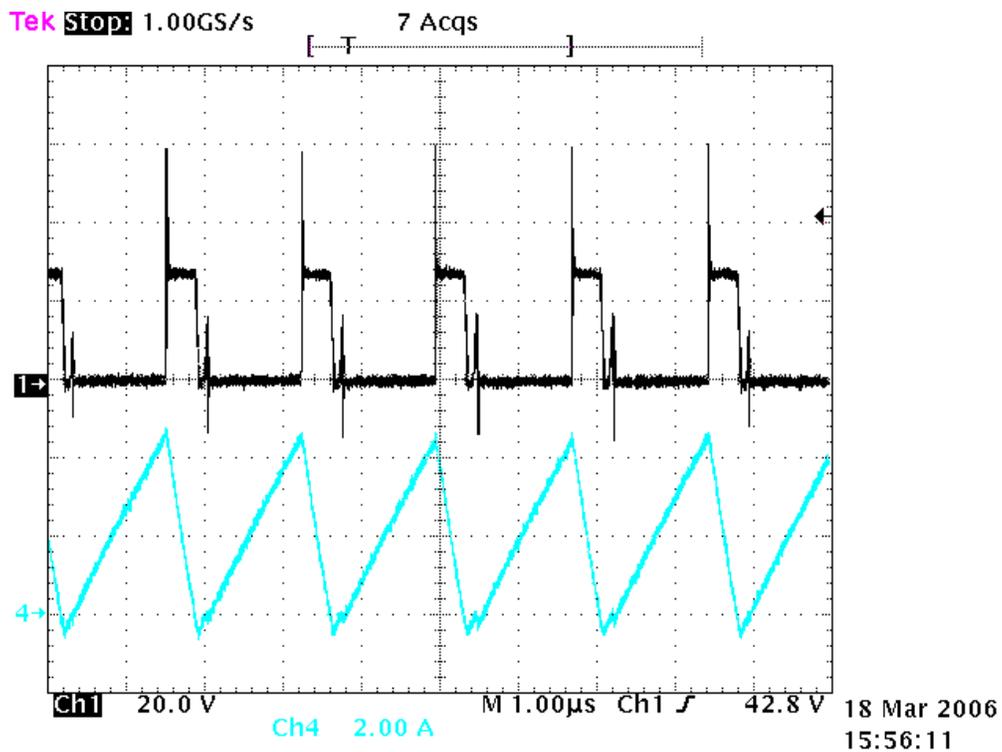


Figure 8- Converter waveforms at $V_{\text{IN}}=7\text{V}$, $I_{\text{out}}=500\text{mA}$, $\text{Ch1}=\text{SWN}$, $\text{Ch4}=\text{IL}$

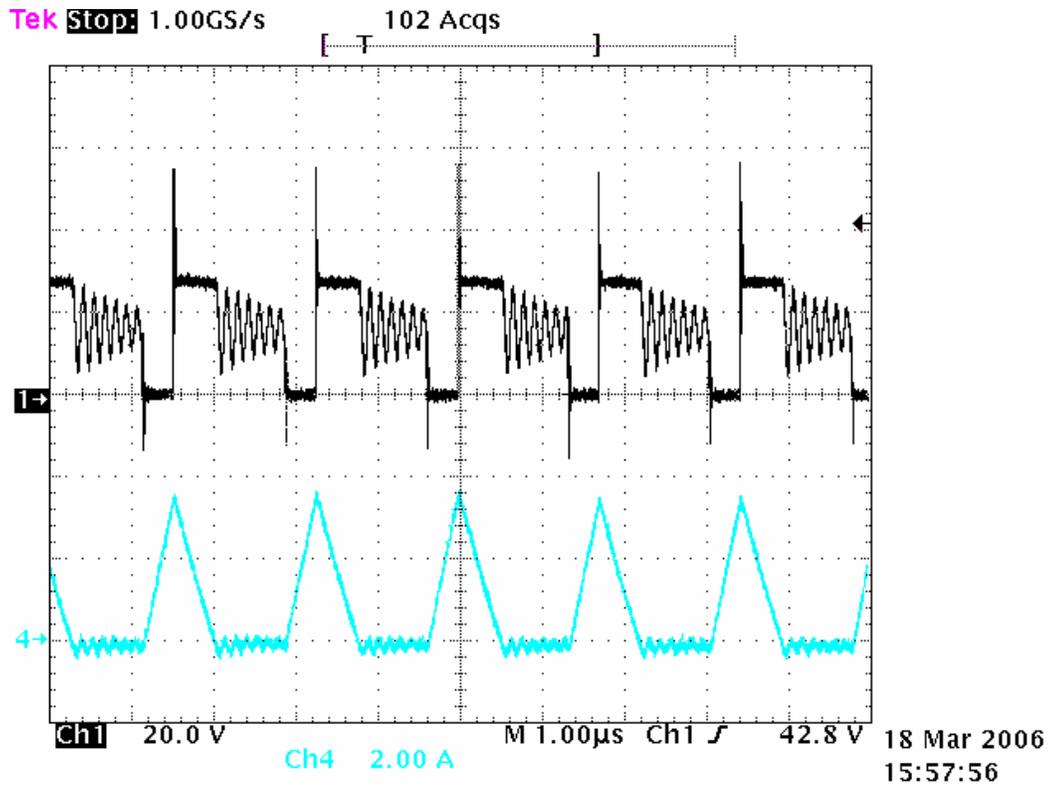


Figure 9- Converter waveforms at $V_{in}=18V$, $I_{OUT}=500mA$, Ch1=SWN, Ch4=IL

Appendix 1: Calculation of Boost converter Control-to-Output transfer function

The following equations can be used to calculate the DC gain and corner frequency of a boost converter's Control-to-Output transfer function [2]

Calculate the pole's corner frequency (f_p) from:

$$f_p = \frac{(2 \times M) - 1}{2 \times \pi \times (M - 1) \times R \times C}$$

where:

$$M = \frac{V_{out}}{V_{in}}$$

$$R = \frac{V_{out}}{I_{out}}$$

C = output capacitance

Calculate the DC gain from:

$$G_{dc} = \left[\frac{2 \times V_{out}}{D} \right] \times \left[\frac{M - 1}{(2 \times M) - 1} \right]$$

Where :

D is steady state duty cycle

$$M = \frac{V_{out}}{V_{in}}$$

Calculate D from:

$$D = \sqrt{\frac{2 \times L}{R_e \times T}}$$

Where:

L is output inductance

T is switching period (1/f)

R_e is the effective resistance of the small signal model of converter

Calculate R_e from:

$$R_e = \frac{V_{in}^2}{I_{out} \times (V_{out} - V_{in})}$$

[2]- *Fundamentals of Power Electronics, Robert Erickson, page 389*